INDEX

Application Notes and Technical Papers

(Arranged Numerically)

APPLICATION NOTES-NUMERIC LISTING — October 1967

APP-41	Stable Wideband Emitter Followers - Paul J. Bénetéau
APP-59	An Improved Emitter-Coupled Multivibrator - P. J. Bénetéau and A. Evangeliste
APP-61/2	Long Delay Transistor Timer - P. Alderisio
APP-64	Application of Milliwatt Micrologic® Elements - H. T. Chua
APP-74	Silicon Transistor Portable TV Receiver - Thomas E. Mills
APP-76	A Transistor Video Amplifier for Radar Display - Samuel Schwartz
APP-77	Transistor Range Marker and Sweep Generator for Radar Display - Samuel Schwartz
APP-81	The Complete X-Band Navigational Radar Set - W. O. Hamlin
APP-85	Micrologic® Shift Counters - George Powers
APP-87	A Varactor Bias Servo System - Bruce O. Anderson
APP-88	Medium Power Silicon Transistor DC to DC Converters - Thomas B. Mills
APP-93	Transient Response Characteristics of Phototransistors - George T. Daughters
APP-103	Applications of the Silicon Planar* Field-Effect Transistor - Larry Blaser and John MacDougall
APP-105	A Monolithic Operational Amplifier - Robert Widlar
APP-106	Using Fairchild Integrated Circuits as Monostable Multivibrators - Robert Ricks
APP-107	Diode Transistor Micrologic® - George Powers
APP-109	Applications of the Silicon Planar* II MOS FET - John MacDougall
APP-111	The Improved μA702**Wideband DC Amplifier - Robert Widlar
APP-112	The Measurement of Transistor Small-Signal Y Parameters - G. Faini, G. Rescio, and G. Riva
APP-114	μA702** Circuit Design Ideas - (Six Authors)
APP-115	Maximum Integrated Circuit Utilization Through Mixing Compatible Logic Families - Robert Ricks
APP-116	The Operation and Use of a Fast Integrated Circuit Comparator - Robert Widlar
APP-117	Frequency Compensation Techniques for an Integrated Operational Amplifier - James Giles
APP-118	Counter Micrologic® A New Dimension in Multi-Function Integrated Circuits - George Powers
APP-119	Ways to Increase Speed in Large Count Binary Counters - Jack Irwin
APP-120	Using the J-K Flip-Flop in Small Modulo Counters - Jack Irwin
APP-121	A High-Efficiency Power Supply Using Micrologic® Integrated Circuits - Samuel Schwartz
APP-123	Core Memory Sense Amplifier Designs Using an Integrated Dual Comparator - Robert Widlar
APP-124	Designing with Off-the-Shelf Linear Microcircuits - Robert Widlar and James Giles
APP-125	A Versatile Tester for Linear Integrated Circuits - James Giles
APP-128	Complementary Transistor Micrologic® Integrated Circuits - R. C. Ghest[1]
APP-130	Aids for Digital IC Systems - Murray Siegel and Lee Marley

*Planar is a patented Fairchild Process.

**The μA702 is renumbered the μA702A.

[1] In process of publication and will be available shortly.

APP-131	Transistor-Transistor Micrologic® Integrated Circuits - John Nichols
APP-132	Single-Phase Control for Cycloconverter - Samual Schwartz[1]
APP-133	Precision Electronic Digital Clock Uses IC's - B. Jensen and J. Irwin
APP-134	Effect of Integrated Circuits on Systems -- Comparative Case - Robert Ricks
APP-135	Performance of the μA703 in 100MHz and 200-MHz Amplifiers and 100-MHz Harmonic Mixers - David Bingham
APP-139	Multivibrator-Type Vertical-Deflection Circuit for Television - J. S. MacDougall
APP-141	Transistorized TV Horizontal Driver System - Larry Blaser and Hermann Ebenhoech
APP-142	15-Watt Audio Amplifier with Short-Circuit Protection - Don Smith
APP-143	A Horizontal Oscillator for Transistorized TV Set - Larry Blaser and Hermann Ebenhoech
APP-144	Frequency Synthesizer for 27-MHz Citizens' Band Transceiver - Larry Blaser
APP-145	Color Television Chroma Reference Systems Using the μA703 - Larry Blaser and Norm Sturn
APP-146	Color TV Sound System Using the Fairchild μA703 - Larry Blaser
APP-147	Characterization and Application of μA703 in Four-Stage High-Quality FM IF Amplifier - David Bingham
APP-148	25-Watt Audio Amplifier with Short-Circuit Protection - Derek Bray and Wesley Votipka
APP-149	Semiconductor Circuits for 19-inch Black and White Television Receivers - Derek Bray
APP-150	Semiconductor Circuits for Hybrid Color Television - Derek Bray
APP-151	High-Performance Integrated FM IF Strips - Ted Hanna
APP-152	250-MHz Distributed Amplifier Suitable for CATV Truck Line - Larry Blaser and Norman Sturn
APP-153	Logic Designs Using the TTμL9008 - Clive Ghest
APP-154	Compatible Current Sinking Logic - Abe Marder and Ralph Bennett
APP-155	Industrial Code Conversion - Don Femling
APP-156	Designing with the μA703 Monolithic RF-IF Amplifier - G. J. Estep
APP-157	A Fixed-Gain Low-Distortion AF Amplifier - G. J. Estep[1]
APP-158	Two-High-Performance Monolithic Microcircuits for FM Sound System - David Bingham
APP-159	A Low-Cost AM-FM Radio Employing an Integrated Circuit Design - David Bingham and John (Ted) Hanna[1]

[1] In process of publication and will be available shortly

APPLICATION NOTES/TECHNICAL PAPERS, NUMERIC LISTING (cont'd)

TP-24	Overloading and Spurious Responses In Transistor FM Tuners - Earl Cummins
TP-27	Forward AGC Design Considerations in Transistorized Television Receivers - Harry Suzuki
TP-28	Measurement of Transistor High-Frequency Current Gain - Heitor Franco
TP-31	An FM Tuner Using MOS-FET'S and Integrated Circuits - John Barrett, Larry Blaser, and Harry Suzuki
TP-32	A Unique Circuit Design for a High-Performance, Operational Amplifier Especially Suited to Monolithic Construction Robert Widlar
TP-33	Some Circuit Design Techniques for Linear Integrated Circuits - Robert Widlar
TP-35	A Black and White and Color TV Video I-F Output Transistor - Derek Bray and Philip Froess
TP-36	A Low Noise, AGC Silicon Transistor Useful From LF to UHF - David Bingham, Harry Suzuki, and Charles Watson
TP-37	Integrated Circuits in Industrial Control - Donald Femling and Jack Irwin
TP-38	Semiconductor Video Amplifiers for Monochrome and Color Receivers - Derek Bray
TP-39	A New 400-Volt Horizontal Output Transistor - T. B. Mills and E. F. Kiburis
TP-40	Radiation Testing of Linear Microcircuits - J. Darryl Lieux
TP-42	Novel Multi-Purpose LIC's Introduce New Concepts into Circuit Design - David Bingham[1]
TP-43	Color TV Processing Using Integrated Circuits - Larry Blaser and Derek Bray

Note: The following publications are obsolete and out of print:
APP's 1-40, 42-45, 48-58, 60, 62, 63, 65-84, 86, 89-92, 94-102, 104, 108, 110, 112, 113, 122, 126, 127, 129, 138, 140. TP's 1-23, 25, 26, 29, 30, 34.

TP-41 is unassigned.

[1] In process of publication and will be available shortly.

COPYRIGHT FAIRCHILD SEMICONDUCTOR 1967 PRINTED U.S.A. 2320-1013-97